



BALUCHISTAN UNIVERSITY OF ENGINEERING AND TECHNOLOGY KHUZDAR

DEPARTMENT: EED EXAMINATION: Final Term 2021

SUBJECT: Electrical Network Analysis CODE: EE- 211

SEMESTER: B.E(3rd Semester) Max: Marks: 50

Time Allowed: 2 hour : 20 minutes

Note: Attempt All questions

Q.NO	Description	Marking Scheme	CLO / PLO	Bloom
1.	Explain the difference between Impedance and Admittance. Find the current and the voltages across each element in Figure 1. Express each quantity also in polar form.	10	CLO-2 PLO-2	C-3
2.	State and explain the term Resonance, resonant frequency and prove that $X_L = X_C$. Determine the Conductance, Capacitive Susceptance, Inductive Susceptance, Total Admittance and Total Impedance of Figure 2.	10	CLO-2 PLO-2	C-3
3.	Define and draw the Step Signal, Impulse Signal and Exponential Decaying Signal. Find the Laplace Transform of the signal $f(t) = \{e^{5t} * e^{2t} * e^{3t} * e^{-5t}\}$	10	CLO-1 PLO-2	C-1
4.	Find the $v_o(t)$ in the circuit of Figure 3, assuming zero initial conditions	10	CLO-1 PLO-2	
5.	State and explain the Z-parameters with basic equations, also Find the Z-parameters of the circuit given in Figure 4	10	CLO-2 PLO-2	C-3

THE END

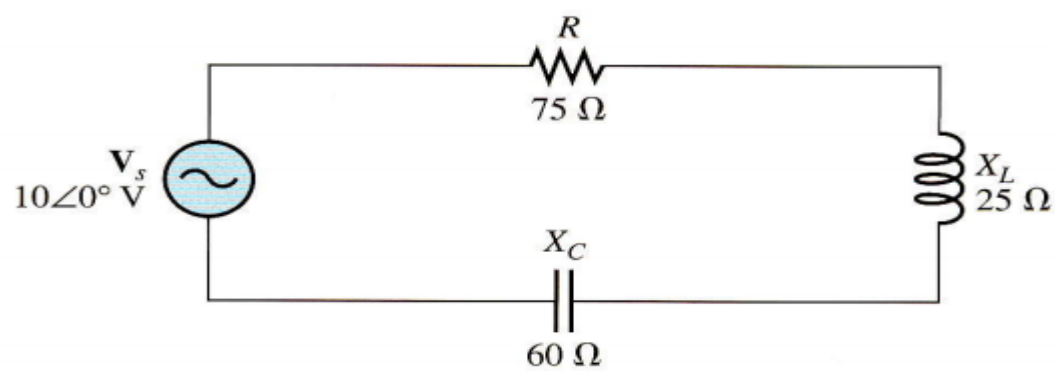


Figure 1

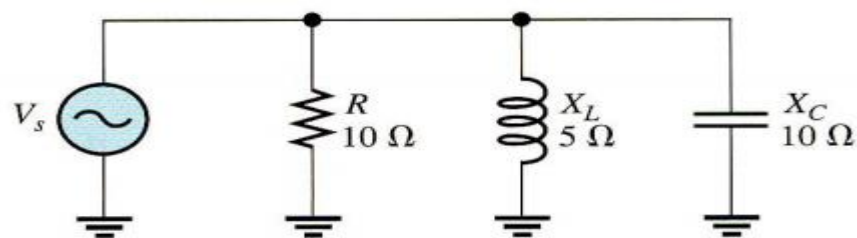


Figure 2

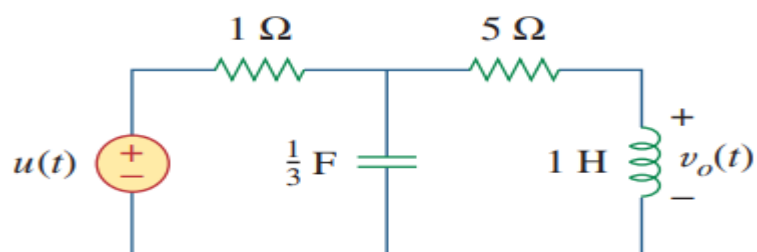


Figure 3

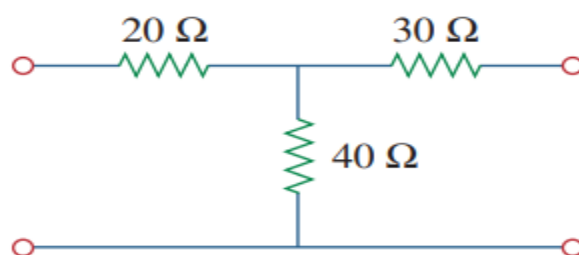


Figure 4